$$\Delta V_1$$

$$\Delta V_2$$

$$\Delta V_3$$

$$\Delta V_1 + \Delta V_3 = 0$$

$$\Delta V_1 + \Delta V_2 = 0$$

$$-\Delta V_2 + \Delta V_3 = 0$$